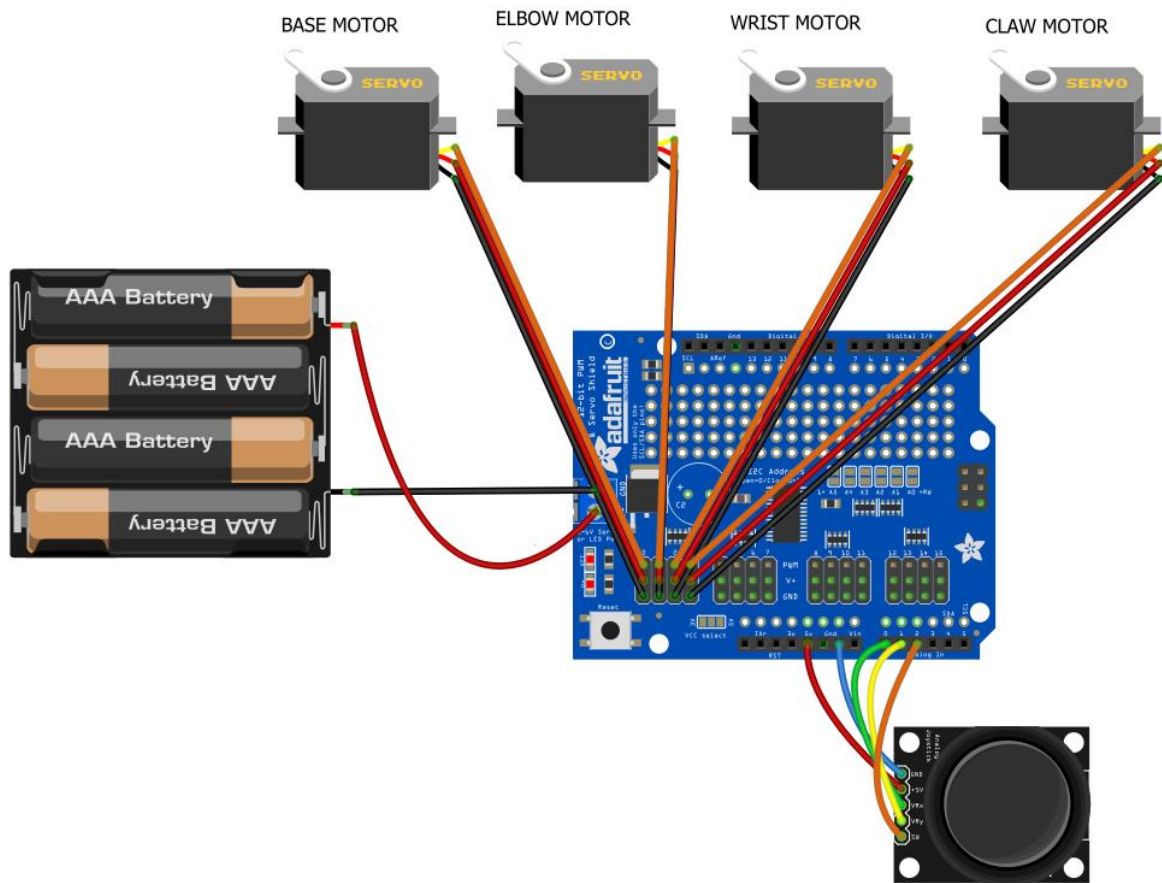





Completed wiring

Step 1

Disconnect the MCU from USB port


Wiring the joystick to the MCU

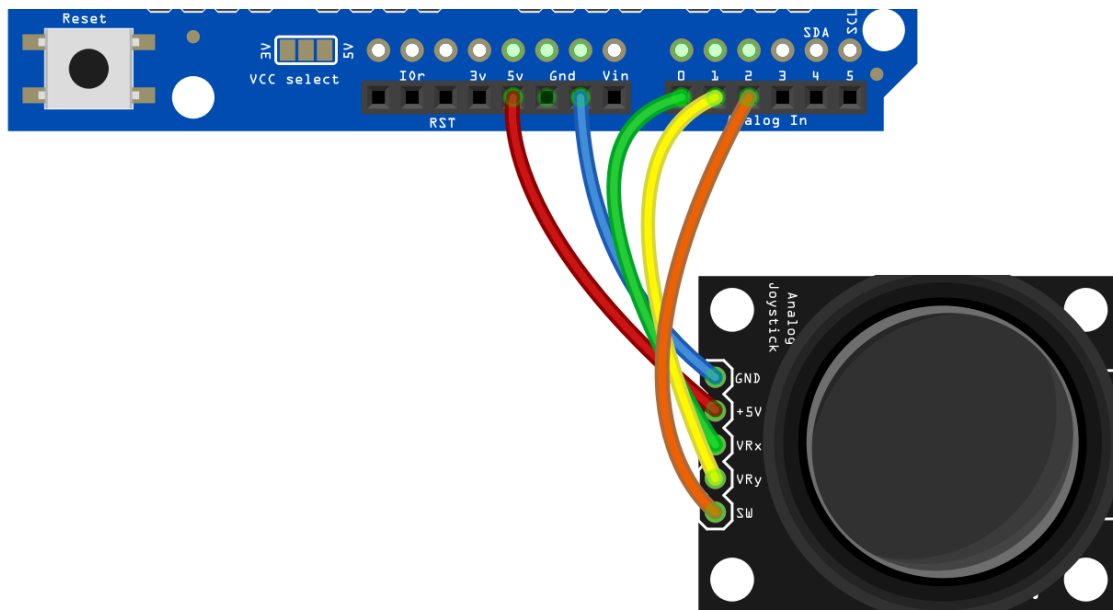

Joystick Pin	MCU Pin
GND	GND
+5v	5v
VRx	A0
VRy	A1
SW	A2

Step 2

Wire the motors

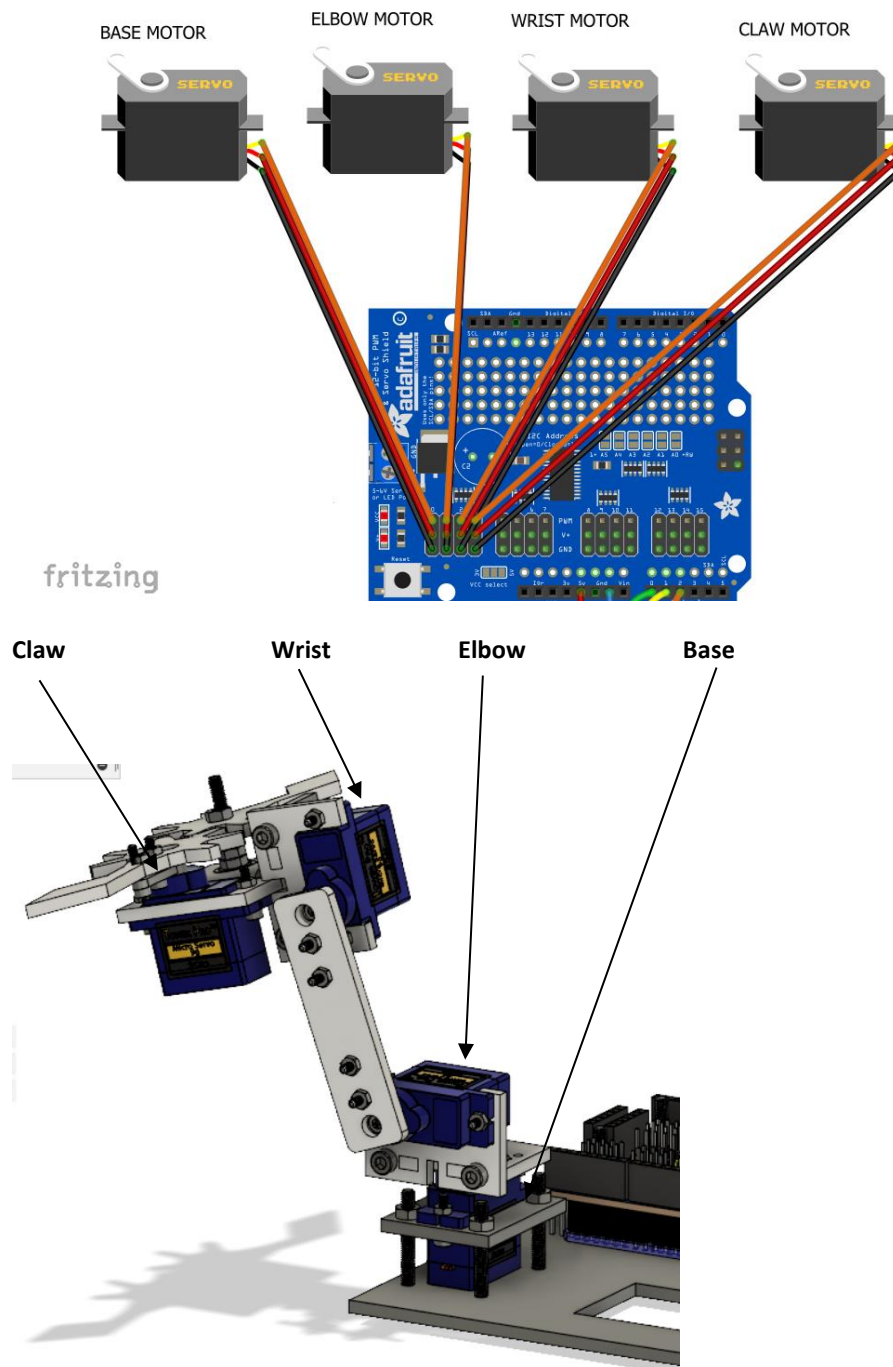

Step Wire Battery

Warning, do not wire incorrectly!

